

MUX, DMUX, Encoder,
Decoder, priority encoder

Digital System Design


Multiplexers and Demultiplexers,
and
Encoders and Decoders

Multiplexers


Multiplexers

- A multiplexer has
 - N control inputs
 - 2^N data inputs
 - 1 output
- A multiplexer routes (or connects) the selected data input to the output.
 - The value of the control inputs determines the data input that is selected.

Multiplexers

 


Multiplexers

 

A	B	F
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

$$Z = A'.B'.I_0 + A'.B.I_1 + A.B'.I_2 + A.B.I_3$$


Multiplexers

 

A	B	C	F
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7

$$Z = A'.B'.C'.I_0 + A'.B'.C.I_1 + A'.B.C'.I_2 + A'.B.C.I_3 + A.B'.C'.I_4 + A.B'.C.I_5 + A.B.C'.I_6 + A.B.C.I_7$$

Multiplexers

 

Multiplexers

Exercise:


Design an 8-to-1 multiplexer using 4-to-1 and 2-to-1 multiplexers only.

Multiplexers

Exercise:

Design a 16-to-1 multiplexer using
4-to-1 multiplexers only.

Multiplexer (Bus)

 


Demultiplexers

Demultiplexers

- A demultiplexer has
 - N control inputs
 - 1 data input
 - 2^N outputs
- A demultiplexer routes (or connects) the data input to the selected output.
 - The value of the control inputs determines the output that is selected.
- A demultiplexer performs the opposite function of a multiplexer.

Demultiplexers

 

$$W = A'.B'.I$$

$$X = A.B'.I$$

$$Y = A'.B.I$$

$$Z = A.B.I$$

A	B	W	X	Y	Z
0	0	I	0	0	0
0	1	0	I	0	0
1	0	0	0	I	0
1	1	0	0	0	I


Decoders

Decoders


- A decoder has
 - N inputs
 - 2^N outputs
- A decoder selects one of 2^N outputs by decoding the binary value on the N inputs.
- The decoder generates all of the minterms of the N input variables.
 - Exactly one output will be active for each combination of the inputs.

What does “active” mean?

Decoders

 

Decoders

 

$$W = (A'.B')'$$

$$X = (A.B')'$$


$$Y = (A'.B)'$$

$$Z = (A.B)'$$


Active-low outputs

A	B	W	X	Y	Z
0	0	0	1	1	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	1	1	1	0

Decoders

 


Decoder with Enable

 

	En	A	B	W	X	Y	Z
enabled	1	0	0	1	0	0	0
	1	0	1	0	1	0	0
	1	1	0	0	0	1	0
	1	1	1	0	0	0	1
disabled	0	x	x	0	0	0	0

Decoder with Enable

 

	En	A	B	W	X	Y	Z
enabled	0	0	0	1	0	0	0
	0	0	1	0	1	0	0
	0	1	0	0	0	1	0
	0	1	1	0	0	0	1
disabled	1	x	x	0	0	0	0

Decoders

Exercise:


Design a 4-to-16 decoder using
2-to-4 decoders only.

Encoders

Encoders

- An encoder has
 - 2^N inputs
 - N outputs
- An encoder outputs the binary value of the selected (or active) input.
- An encoder performs the inverse operation of a decoder.
- Issues
 - What if more than one input is active?
 - What if no inputs are active?

Encoders

 


A	B	C	D	Y	Z
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

Priority Encoders

- If more than one input is active, the higher-order input has priority over the lower-order input.
 - The higher value is encoded on the output
- A valid indicator, d , is included to indicate whether or not the output is valid.
 - Output is invalid when no inputs are active
 - $d = 0$
 - Output is valid when at least one input is active
 - $d = 1$

Why is the valid indicator needed?

Priority Encoders

 

y_0	y_1	y_2	y_3	y_4	y_5	y_6	y_7	a	b	c	d
0	0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
X	1	0	0	0	0	0	0	0	0	1	1
X	X	1	0	0	0	0	0	0	1	0	1
X	X	X	1	0	0	0	0	0	1	1	1
X	X	X	X	1	0	0	0	1	0	0	1
X	X	X	X	X	1	0	0	1	0	1	1
X	X	X	X	X	X	1	0	1	1	0	1
X	X	X	X	X	X	X	1	1	1	1	1

Designing logic circuits using multiplexers

Using an n -input Multiplexer

- Use an n -input multiplexer to realize a logic circuit for a function with n minterms.
 - $m = 2^n$, where $m = \#$ of variables in the function
- Each minterm of the function can be mapped to an input of the multiplexer.
- For each row in the truth table, for the function, where the output is 1, set the corresponding input of the multiplexer to 1.
 - That is, for each minterm in the minterm expansion of the function, set the corresponding input of the multiplexer to 1.
- Set the remaining inputs of the multiplexer to 0.

Using an n -input Mux

Example:

Using an 8-to-1 multiplexer, design a logic circuit to realize the following Boolean function

$$F(A,B,C) = \Sigma m(2, 3, 5, 6, 7)$$

Using an n -input Mux

Example:

Using an 8-to-1 multiplexer, design a logic circuit to realize the following Boolean function

$$F(A,B,C) = \Sigma m(1, 2, 4)$$

Using an $(n / 2)$ -input Multiplexer


- Use an $(n / 2)$ -input multiplexer to realize a logic circuit for a function with n minterms.
 - $m = 2^n$, where $m = \#$ of variables in the function
- Group the rows of the truth table, for the function, into $(n / 2)$ pairs of rows.
 - Each pair of rows represents a product term of $(m - 1)$ variables.
 - Each pair of rows can be mapped to a multiplexer input.
- Determine the logical function of each pair of rows in terms of the m^{th} variable.
 - If the m^{th} variable, for example, is x , then the possible values are x , x' , 0, and 1.

Using an $(n / 2)$ -input Mux

Example: $F(x,y,z) = \Sigma m(1, 2, 6, 7)$

x	y	z	F	
0	0	0	0	$F = z$
0	0	1	1	
0	1	0	1	$F = z'$
0	1	1	0	
1	0	0	0	$F = 0$
1	0	1	0	
1	1	0	1	$F = 1$
1	1	1	1	

(a) Truth table

 


(b) Multiplexer implementation

Using an $(n / 2)$ -input Mux

Example: $F(A,B,C,D) = \Sigma m(1,3,4,11,12-15)$

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>F</i>	
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = D'$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	

 

Using an $(n / 4)$ -input Mux

The design of a logic circuit using an $(n / 2)$ -input multiplexer can be easily extended to the use of an $(n / 4)$ -input multiplexer.

Designing logic circuits using decoders

Using an n -output Decoder

- Use an n -output decoder to realize a logic circuit for a function with n minterms.
- Each minterm of the function can be mapped to an output of the decoder.
- For each row in the truth table, for the function, where the output is 1, sum (or “OR”) the corresponding outputs of the decoder.
 - That is, for each minterm in the minterm expansion of the function, OR the corresponding outputs of the decoder.
- Leave remaining outputs of the decoder unconnected.

Using an n -output Decoder

Example:

Using a 3-to-8 decoder, design a logic circuit to realize the following Boolean function

$$F(A,B,C) = \Sigma m(2, 3, 5, 6, 7)$$

Using an n -output Decoder

Example:

Using two 2-to-4 decoders, design a logic circuit to realize the following Boolean function

$$F(A,B,C) = \Sigma m(0, 1, 4, 6, 7)$$

Questions?